سوال ۸)

مداری برای مدیریت پارکینگ دانشگاه طراحی کنید که امکانات زیر را داشته باشد:

- ۱) اولویت فضای پارکینگ با اساتید و کارمندان دانشگاه است و این ظرفیت بر اساس آمار حداکثر ۵۰۰ خودرو تعیین گردیده است.
 - ۲) باتوجهبه اینکه فضای کل پارکینگ ۲۰۰ خودرو است از ساعت ۸ تا ۱۳ فقط ۲۰۰ ظرفیت خالی برای ورود آزاد موجود است.
- ۳) از ساعت ۱۳ تا ۱۶ به ازای هر ساعت ظرفیت ورود آزاد ۵۰ خودرو افزایش می یابد و در ساعت ۱۶ ظرفیت ورود آزاد به ۵۰۰
 خودرو می رسد.

الف) اگر در هنگام ورود/خروج خودرو یک سیگنال ورودی به مدار نوع آن را مشخص کند (دانشگاه/آزاد): با زبان وریلاگ مداری را توصیف کنید که دارای ورودیها/خروجیهای زیر باشد:

خروجىها					
uni_parked_car	تعداد خودروهایی متعلق به دانشگاه که در پارکینگ پارک شدهاند.				
parked_care	تعداد خودروهای پارک شده در پارکینگ مربوط به ظرفیت آزاد				
uni_vacated_space	تعداد فضای خالی متعلق به دانشگاه				
vacated_space	تعداد فضاهای خالی مربوط به ظرفیت آزاد				
uni_is_vacated_space	آیا فضای خالی برای دانشگاه موجود است؟				
is_vacated_space	آیا فضای خالی برای ظرفیت آزاد موجود است؟				
	ورودىها				
car_entered	ورود یک خودرو				
is_uni_car_entered	آیا خودرو وارد شده متعلق به دانشگاه است؟				
car_exited	خروج یک خودرو				
is_uni_car_ exited	آیا خودرو خارج شده متعلق به دانشگاه است؟				

درصورتیکه نیاز به ورودیها/خروجیهای دیگری هم است آن را با ذکر دلیل به طراحی خود بیفزایید و جهت اطمینان از صحت عملکرد مدار، مدار خود را مورد آزمون قرار دهید (۵۰ نمره).

ب) مدار خود را برای یک FPGA به انتخاب خود سنتز کنید. از گزارشهای سنتز، بیشترین فرکانس ممکن برای این مدار را با ذکر دلیل مشخص کنید (۱۰ نمره).

الف)

برای محاسبه زمان من مدول Counter را طراحی کردم که این مدول پارامتر n را

میگیرد (که مشخص کننده این است که هر چند کلاک را معادل یک ساعت میداند).

و همچنین سیگنال ورودی clk و سیگنال خروجی hour و سیگنال count که در واقع به

نو عی نشان دهنده دقیقه هست بر ای Counter است.

با متغیر count تعداد کلاک های گذشته را میشماریم و اگر برابر با پارامتر n شد سیگنال hour را فعال میکنیم و در بقیه حالات hour را با 0 مقداردهی میکنیم.

من هر 60 كلاك را معادل گذشت يك ساعت ميدانم.

```
module Counter #(parameter n = 60) (input clk, output reg hour,output reg[6:0] count);

initial begin
hour = 0;
count = 0;
end

always @(posedge clk) begin
count <= count + 1;
if (count % (n-1) == 0 && count!=0)begin
hour <= 1;
count <= 0;
end

else
hour <= 0;
end
end
end
end
endmodule</pre>
```

سپس مدول Parking را طبق خواسته سوال ایجاد کردم و سپس همانطوری که سوال از ما خواسته ورودی ها و خروجی های مدنظر را در پورت های مناسب قرار دادم و از طرفی برای اعداد ۲۰۰ و ۵۰۰ همان ۹ بیت کافی است. و همینطور ورودی کلاک را نیز برای مدول Parking در نظر گرفتم و از طرفی ورودی و خروجی در صورت سوال را نیز در پورت های مناسب قرار دادم. موضوع دیگر در مورد مقدار ساعت و دقیقه است که برای نمایش ساعت و دقیقه به ترتیب سیگنال های timer_counter و timer_hour را تعریف کردم.

برای نگه داری حداکثر ظرفیت آزاد و دانشگاه دو متغیر university_capacity و public_capacity را تعریف کردیم و برای مقدار دهی اولیه دلخواه به آنها از تعریف پارامتر استفاده کردیم.

```
و همچنین برای اینکه بفهمیم ساعت بعدی فرا رسیده از سیگنال hour استفاده میکنیم ( که به مدول Counter و صل است ).
```

مقدار دهی های اولیه را مطابق خواسته سوال در یک بلاک initial انجام میدهیم.

قسمت پورت و مقدار دهی اولیه سیگنال های خروجی و سیگنال های داخلی به شرح زیر

است:

```
module Parking #(parameter uni_vacated_space_initial=500, parameter time_initial=8,parameter university_capacity_initial=500,
parameter vacated_space_initial=200,parameter public_capacity_initial=200)
(input car_entered, is_uni_car_entered, car_exited, is_uni_car_exited, clk,
    output req uni_is_vacated_space, is_vacated_space,
    output reg [9:0] uni_parked_car, parked_car, uni_vacated_space, vacated_space,output wire [6:0]time_counter,output reg[4:0] timer_hour);
    reg [9:0] university_capacity;
    wire hour;
    req [9:0] public_capacity;
    reg [9:0] changed_capacity;
        parked_car = 0;
        uni_vacated_space = uni_vacated_space_initial;
        timer_hour= time_initial;
        uni_parked_car = 0;
        university_capacity = university_capacity_initial;
        vacated_space = vacated_space_initial;
        public_capacity = public_capacity_initial;
```

خب حالا به سراغ توضیح مدول parking و نحوه عملکرد آن میرویم: در این قسمت یک نکته کلیدی وجود دارد و آن هم این است که همواره اولویت با پرسنل دانشگاهی است. به این معنا که اگر قرار بر اضافه کردن ظرفیت به قسمت آزاد باشد اگر به اندازه سقف تعیین شده جای خالی باشد همان مقدار و گرنه به اندازه ظرفیت خالی اضافه میکنیم.

نکته دیگر در مورد اضافه کردن ظرفیت است که چون از ساعت ۱۳ به بعد به ازای گذشت هر یک ساعت ما ظرفیت های آزاد را زیاد میکنیم پس فقط به ازای ساعات ۱۴ و ۱۵ ظرفیت تا حداکثر ۵۰ تا زیاد میشود و همچنین در ساعت ۱۶ نیز باید ظرفیت را با توجه به اینکه دانشگاه اولویت دارد زیاد کنیم. مثلا ببینیم آیا فضای خالی که از دانشگاه باقی مانده به اندازه ای است که بتوان ظرفیت آزاد را تا 500 تا افزایش داد.

```
always @(posedge hour or posedge clk) begin

if (hour) begin

timer_hour = timer_hour + 1;

if (timer_hour % 24 == 14 || timer_hour % 24 == 15) begin

changed_capacity = (uni_vacated_space < 50) ? uni_vacated_space : 50;

university_capacity = university_capacity;

uni_vacated_space = uni_vacated_space - changed_capacity;

public_capacity = public_capacity + changed_capacity;

vacated_space = vacated_space + changed_capacity;

end else if (timer_hour % 24 == 16) begin

university_capacity = (uni_parked_car > 200) ? uni_parked_car : 200;

public_capacity = 700 - university_capacity;

vacated_space = public_capacity - parked_car;

uni_vacated_space = university_capacity - uni_parked_car;

end

end

end

end else if (clk) begin
```

بخش مربوط به ورود ماشین و تغییر ظرفیت آزاد و دانشگاهی نیز که با سیگنال clk کار میکند به شکل زیر میباشد:

```
uni_is_vacated_space = (uni_vacated_space != 0) ? 1 : 0;
is_vacated_space = (vacated_space != 0) ? 1 : 0;
if (car_entered && is_uni_car_entered && uni_is_vacated_space ) begin
    uni_parked_car = uni_parked_car + 1;
    uni_vacated_space = uni_vacated_space - 1;
end else if (car_entered && !is_uni_car_entered && is_vacated_space) begin
    parked_car = parked_car + 1;
    vacated_space = vacated_space - 1;
end else if (car_exited && is_uni_car_exited && uni_parked_car > 0 ) begin
    uni_parked_car = uni_parked_car - 1;
    uni_vacated_space = uni_vacated_space + 1;
end else if (car_exited && !is_uni_car_exited && parked_car > 0) begin
    parked_car = parked_car - 1;
    vacated_space = vacated_space + 1;
if(timer_hour%24==0)
    timer_hour=0;
```

در این قسمت نیز مجددا بحث اولویت ها و اینکه من باید ببینم اصلا ظرفیت دارم که ماشین اضافه کنم را مشاهده میکنیم و یه موضوع دیگر این که برای من در موقع تست گرفتن پیش آمد این بود که ممکن است سیگنال خروج ماشین زیاد فعال بماند و تعداد ماشین های باقی مانده به حدی کم شود که عدد حاصل منفی شود و من از این رو، شرط مثبت بودن تعداد ماشین های پارک شده را چک کردم. نکته دیگر چون من میخوام ساعت را هم نمایش دهم چک میکنم که اگر ساعت ۲۴ شد، به صفر تغییر کند. حال به سراغ testBench نوشتن میرویم. تست بنج من به شکل زیر است و خروجی های آن نیز در فایل output.txt آورده شده است:

```
module Parking_TB();
    reg car_entered, is_uni_car_entered, car_exited, is_uni_car_exited,clk;
    wire uni_is_vacated_space, is_vacated_space;
    wire [9:0] uni_parked_car, parked_car, uni_vacated_space, vacated_space;
    wire [6:0]time_counter;
   wire [4:0]time_hour;
       #5 clk = ~clk;
   Parking #(500,8,500,200,200)parking(car_entered, is_uni_car_entered, car_exited, is_uni_car_exited,clk,
   uni_is_vacated_space, is_vacated_space,uni_parked_car, parked_car, uni_vacated_space, vacated_space,time_counter,time_hour);
       car_entered=0;
       is_uni_car_entered=0;
       car_exited=0;
       is_uni_car_exited=0;
       clk=0;
       #20 car_entered = 1;
       #30 is_uni_car_entered = 1;
       #50 car_entered = 0; is_uni_car_entered = 0; car_exited = 1; is_uni_car_exited = 0;
       #50 car_exited = 1; is_uni_car_exited = 1;
       #10000 $finish();
       $monitor("time= %d:%d\n: car_entered = %b || is_uni_car_entered = %b || car_exited = %b || is_uni_car_exited = %b >>>> uni_is_vacated_space = %d ||",
        time_hour,time_counter, car_entered, is_uni_car_entered, car_exited, is_uni_car_exited,uni_is_vacated_space,
         is_vacated_space,uni_parked_car, parked_car, uni_vacated_space, vacated_space);
       $dumpfile("Parking.vcd");
       $dumpvars(0,Parking_TB);
```

بخشی از خروجی این testBench به شکل زیر است:

```
time= 8: 0
: car_entered = 0 || is_uni_car_entered = 0 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = x ||is_vacated_space = x
|| uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 500 || vacated_space = 200
: car_entered = 0 || is_uni_car_entered = 0 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 500 || vacated_space = 200
time= 8: 2
: car_entered = 0 || is_uni_car_entered = 0 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 500 || vacated_space = 200
: car_entered = 1 || is_uni_car_entered = 0 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 500 || vacated_space = 200
time= 8: 3
: car_entered = 1 || is_uni_car_entered = 0 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 0 || parked_car = 1 || uni_vacated_space = 500 || vacated_space = 199
: car_entered = 1 || is_uni_car_entered = 0 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
|| uni_parked_car = 0 || parked_car = 2 || uni_vacated_space = 500 || vacated_space = 198
time= 8: 4
: car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 0 || parked_car = 2 || uni_vacated_space = 500 || vacated_space = 198
: car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 1 || parked_car = 2 || uni_vacated_space = 499 || vacated_space = 198
time= 8: 6
: car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
|| uni_parked_car = 2 || parked_car = 2 || uni_vacated_space = 498 || vacated_space = 198
```

اگر بخواهیم کمی خروجی را تحلیل کنیم تا از عملکرد درست آن مطمئن شویم:

در ساعت ۸ که سیستم شروع به کار میکند باید ظرفیت های دانشگاه و آزاد به ترتیب 500 و 200 باشد که

همانطور که میبینیم اینگونه است.

در ساعت 8:02 یک ماشین آزاد وارد میشود که نتجیتا در کلاک بعدی باید ظرفیت آزاد یکی کم شده باشد، که همینطور نیز است.

این روند ادامه دارد و مدام بر تعداد ماشین های آزاد افزوده میشود تا اینکه در زمان 8:05 نوع این

ماشین عوض میشود و ماشین پرسنلی وارد میشود از این زمان تا ساعت 8:10 مدام ماشین

پرسنلی وارد میشود

```
24 : car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
25 || uni_parked_car = 0 || parked_car = 3 || uni_vacated_space = 500 || vacated_space = 197
26 time= 8: 6
27 : car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
28 || uni_parked_car = 1 || parked_car = 3 || uni_vacated_space = 499 || vacated_space = 197
29 time= 8: 7
30 : car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
31 || uni_parked_car = 2 || parked_car = 3 || uni_vacated_space = 498 || vacated_space = 197
32 time= 8: 8
33 : car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
34 || uni_parked_car = 3 || parked_car = 3 || uni_vacated_space = 497 || vacated_space = 197
35 time= 8: 9
36 : car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
37 || uni_parked_car = 4 || parked_car = 3 || uni_vacated_space = 496 || vacated_space = 197
38 time= 8: 10
39 : car_entered = 1 || is_uni_car_entered = 1 || car_exited = 0 || is_uni_car_exited = 0 >>>>> uni_is_vacated_space = 1 || is_vacated_space = 1
40 || uni_parked_car = 5 || parked_car = 3 || uni_vacated_space = 495 || vacated_space = 197
```

و همانطور که میبینیم از اینجا به بعد دیگر ماشینی وارد نمیشود و تا ساعت 8:13 ما با خروج ماشین

های آزاد روبرو هستیم.

```
time= 8: 10

time= 8: 11

time= 8: 11

time= 8: 11

time= 8: 11

time= 8: 12

time= 8: 13

time= 8: 13
```

خواهد داشت:

```
time= 8: 15

image: 15

car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1

| || uni_parked_car = 5 || parked_car = 0 || uni_vacated_space = 495 || vacated_space = 200

| || uni_parked_car = 5 || parked_car = 0 || uni_vacated_space = 495 || vacated_space = 200

| || uni_parked_car = 4 || parked_car = 0 || uni_vacated_space = 496 || vacated_space = 200

| || uni_parked_car = 4 || parked_car = 0 || uni_vacated_space = 496 || vacated_space = 200

| || uni_parked_car = 3 || parked_car = 0 || uni_vacated_space = 497 || vacated_space = 200

| || uni_parked_car = 3 || parked_car = 0 || uni_vacated_space = 497 || vacated_space = 200

| || uni_parked_car = 3 || parked_car = 0 || uni_vacated_space = 497 || vacated_space = 200

| || uni_parked_car = 2 || parked_car = 0 || uni_vacated_space = 498 || vacated_space = 200

| || uni_parked_car = 2 || parked_car = 0 || uni_vacated_space = 498 || vacated_space = 200

| || uni_parked_car = 2 || parked_car = 0 || uni_vacated_space = 498 || vacated_space = 200

| || uni_parked_car = 1 || parked_car = 0 || uni_vacated_space = 499 || vacated_space = 200

| || uni_parked_car = 1 || parked_car = 0 || uni_vacated_space = 499 || vacated_space = 200

| || uni_parked_car = 1 || parked_car = 0 || uni_vacated_space = 499 || vacated_space = 200

| || uni_parked_car = 1 || parked_car = 0 || uni_vacated_space = 499 || vacated_space = 200

| || uni_parked_car = 0 || uni_vacated_space = 499 || vacated_space = 200

| || uni_parked_car = 0 || uni_vacated_space = 499 || vacated_space = 200
```

از نكات ديگر طراحي ميتوان به اينكه در ساعت 14 و 15 و 16 بايد ظرفيت آزاد زياد شود اشاره كرد كه در ادامه ميبينيم:

```
554 time= 14: 0
555 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1
556 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 500 || vacated_space = 200
558 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
559 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 450 || vacated_space = 250
561 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
562 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 450 || vacated_space = 250
563 time= 14: 3
564 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
565 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 450 || vacated_space = 250
567 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
568 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 450 || vacated_space = 250
569 time= 14: 5
570 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
571 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 450 || vacated_space = 250
572 time= 14: 6
573 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 ||is_vacated_space = 1
    || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 450 || vacated_space = 250
```

```
time= 15: 0

734 time= 15: 0

735 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1

736 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 400 || vacated_space = 300

737 time= 16: 1

738 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1

739 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 200 || vacated_space = 500

740 time= 16: 2

741 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1

742 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 200 || vacated_space = 500

743 time= 16: 3

744 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1

745 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 200 || vacated_space = 500

746 time= 16: 4

747 : car_entered = 0 || is_uni_car_entered = 0 || car_exited = 1 || is_uni_car_exited = 1 >>>> uni_is_vacated_space = 1 || is_vacated_space = 1

748 || uni_parked_car = 0 || parked_car = 0 || uni_vacated_space = 200 || vacated_space = 500

749 time= 16: 5
```

ب) فایل مربوط به Quartus این پروژه در فولدر پروژه آمده است.

همانطور که در تصویر زیر میبینیم بیشینه فرکانس برابر با 6.46MHz است.

	Fmax	Restricted Fmax	Clock Name	Note
1	6.46 MHz	6.46 MHz	clk	71111
2	134.93 MHz	134.93 MHz	Counter:counter hour	

کردن به گزارش تاخیر مسیر داده ها چک کنیم:

	Slack	From Node	To Node	Launch Clock	Latch Clock	Relationship	Clock Skew	Data Delay
1	-153.895	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.624
2	-153.885	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.614
3	-153.885	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.614
4	-153.885	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.614
5	-153.885	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.614
5	-153.884	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.613
7	-153.884	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.613
8	-153.884	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.613
9	-153.884	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.613
10	-153.883	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.612
1	-153.882	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.611
12	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
13	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
14	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
5	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
6	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
7	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
8	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
9	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
0.0	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
1	-153.875	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.604
2	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
23	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
4	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
5	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
6	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
7	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
8	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
9	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
0	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
1	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
32	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
33	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
34	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603
35	-153.874	Counter:counter count[2]	Counter:counter hour	clk	clk	1.000	0.000	154.603

به طور کلی تاخیر مسیر داده ها برابر با 154ns است و همانطور که میبینیم فرکانس بیشینه تقریبا با

معكوس أن برابر است:

1/154ns~6.49MHz